

1) Resistance total

$$R_T = R_1 + R_2 + R_3$$

$$= 20 + 30 + 50$$

$$= 100 \Omega$$

2) Total current

$$I = \frac{V}{R_T}$$

$$= \frac{125}{100}$$

$$= 1.25$$

$$A$$

$$= 1.25 A$$

3) Current through each resistor

Circuit in series hence current is the same for each resistor.

$$1.25 A$$

4) Voltage drop across each resistor

$$V = IR$$

$$20 \Omega \text{ resistor} = 1.25 \times 20 = 25 V$$

$$30 \Omega \text{ resistor} = 1.25 \times 30 = 37.5 V$$

$$50 \Omega \text{ resistor} = 1.25 \times 50 = 62.5 V$$

5. Power dissipated by each resistor

$$P = VI$$

$$20 \Omega \text{ resistor} = 25 \times 1.25 = 31.25 \text{ W}$$

$$30 \Omega \text{ resistor} = 37.5 \times 1.25 = 46.88 \text{ W}$$

$$50 \Omega \text{ resistor} = 62.5 \times 1.25 = 78.13 \text{ W}$$

CIRCUIT B

1) Total resistance

$$\frac{1}{R_T} = \frac{1}{20} + \frac{1}{100} + \frac{1}{50}$$

$$= 0.05 + 0.01 + 0.02$$

$$= \frac{1}{0.08}$$

$$= 12.5 \Omega$$

2) Total current

$$I = \frac{V}{R_T} = \frac{125V}{12.5 \Omega}$$

$$= 10A$$

3) Current through each resistor

$$20 \Omega \text{ resistor} = \frac{125V}{20 \Omega} = 6.25A$$

$$100 \Omega \text{ resistor} = \frac{125V}{100 \Omega} = 1.25A$$

$$50 \Omega \text{ resistor} = \frac{125V}{50 \Omega} = 2.5A$$

4) Voltage drop across each resistor.

Circuit in parallel so each resistor receives full voltage.

$$V_{20\Omega} = V_{100\Omega} = V_{50\Omega} = 125V$$

5) Power dissipated through each resistor

$$P_{20\Omega} = 125V \times 6.25A = 781.25W$$

$$P_{100\Omega} = 125V \times 1.25A = 156.25W$$

$$P_{50\Omega} = 125V \times 2.5A = 312.5W$$